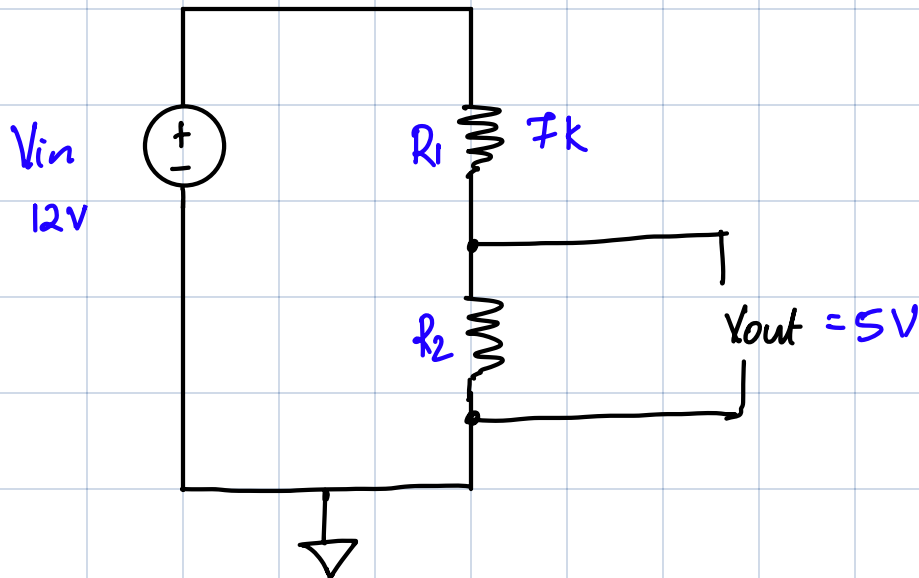


EECE 5685

VIRTUAL LAB #1: LINEAR REGULATOR

Part 1: Resistor Divider



a) given $V_{in} = 12V$
 $R_1 = 7k$
 $V_{out} = 5V$

We know that for a resistor divider circuit $V_{out} = \frac{V_{in} R_2}{R_1 + R_2}$

$$\therefore V_{out} = \frac{12 \times R_2}{7 + R_2}$$



$$5 = \frac{12 R_2}{7 + R_2}$$



$$35 + 5R_2 = 12 R_2$$


$$7R_2 = 35$$

$$R_2 = 35/7$$

$$R_2 = 5k\Omega$$

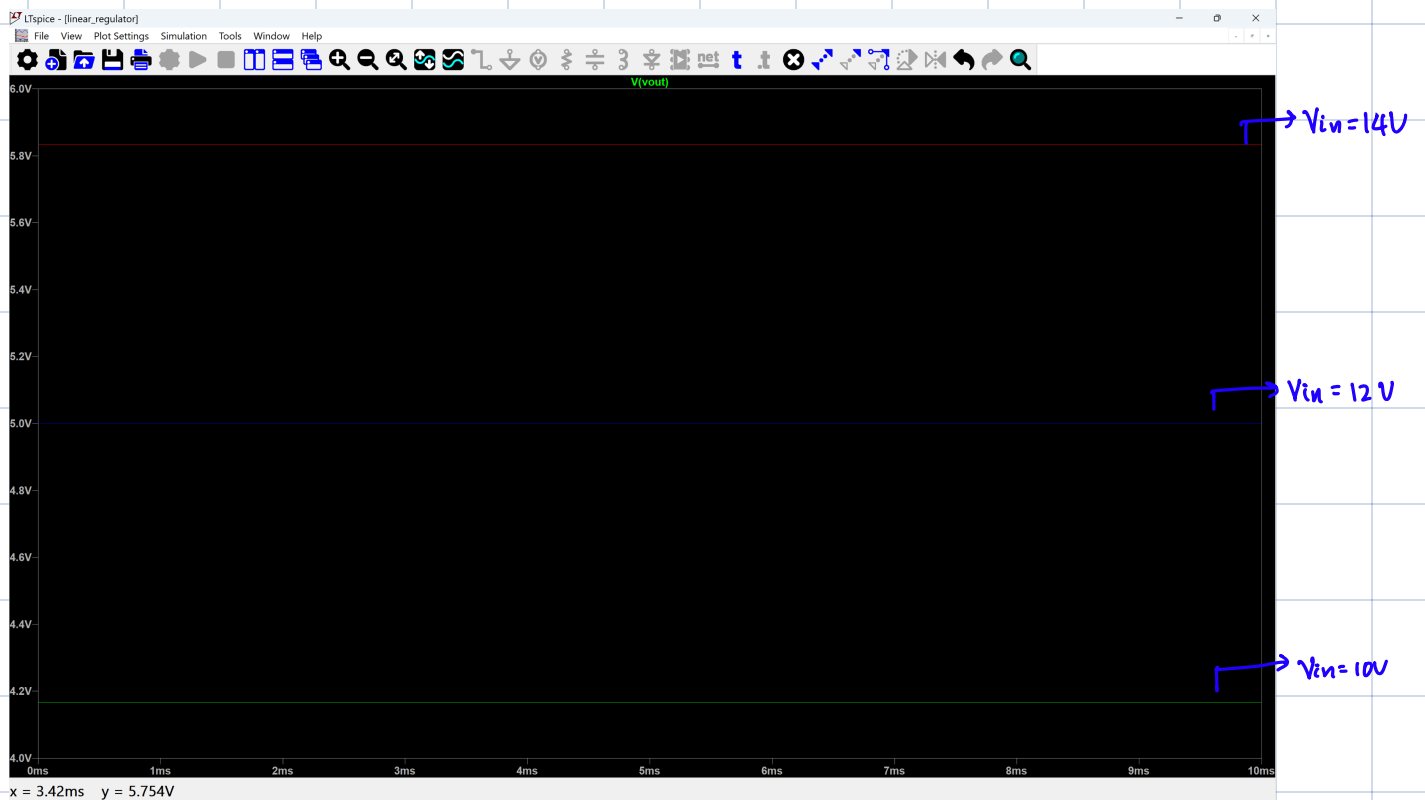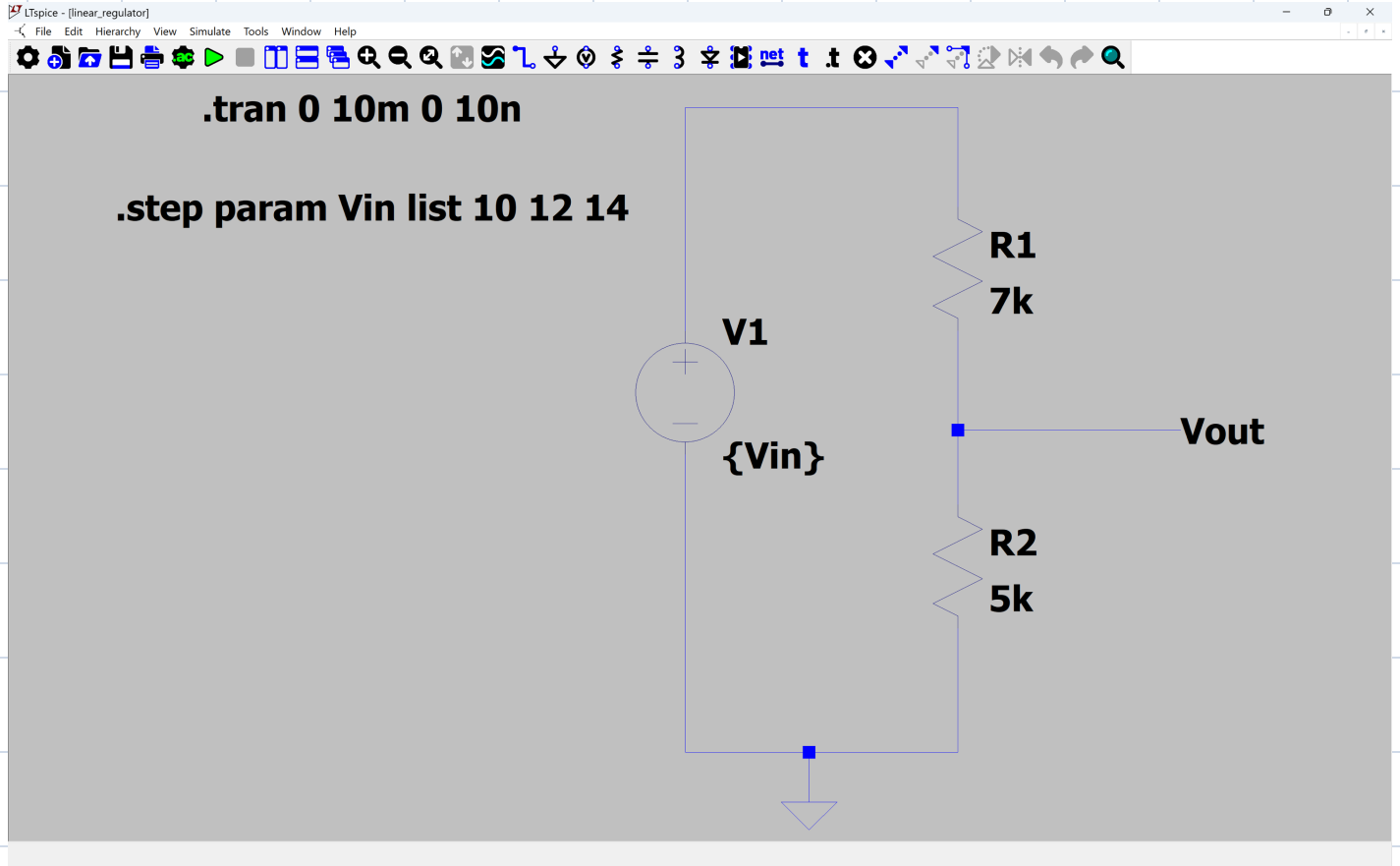


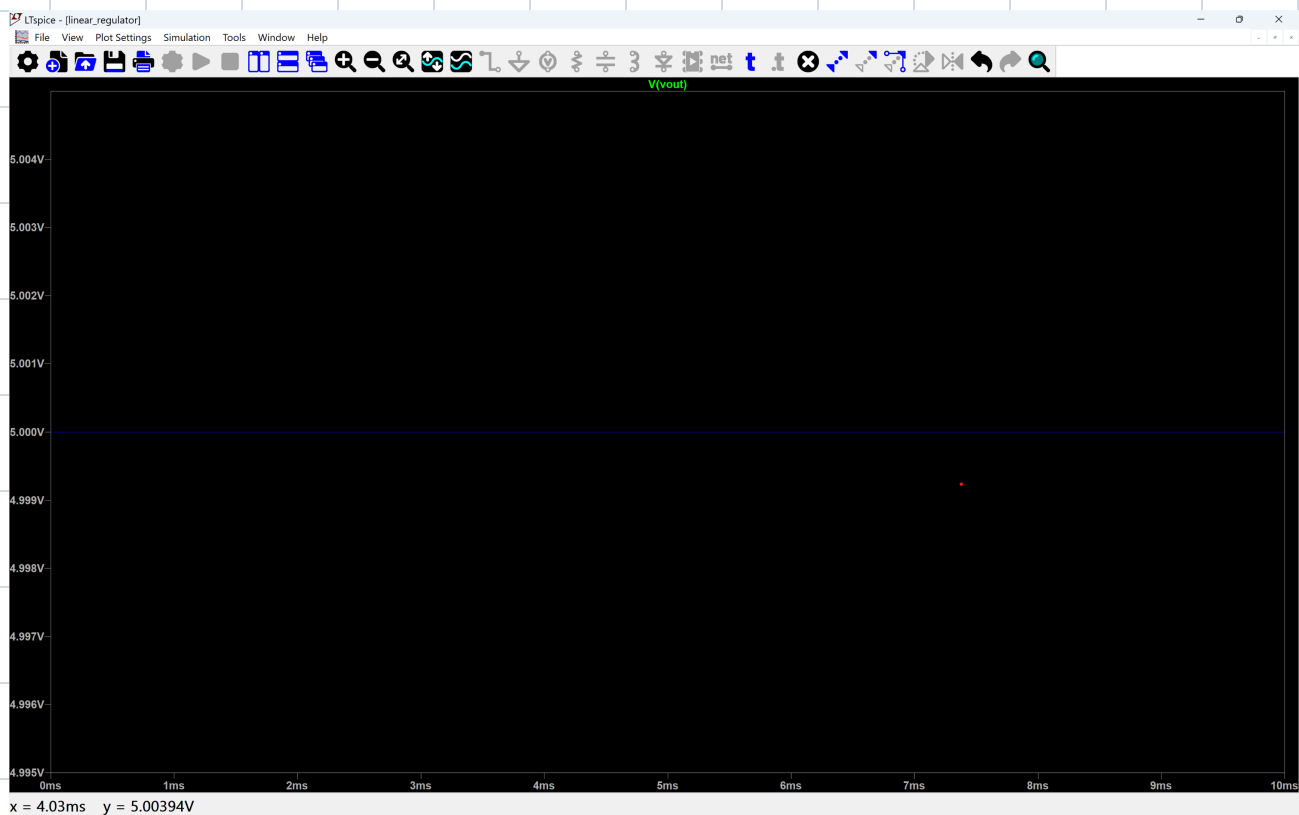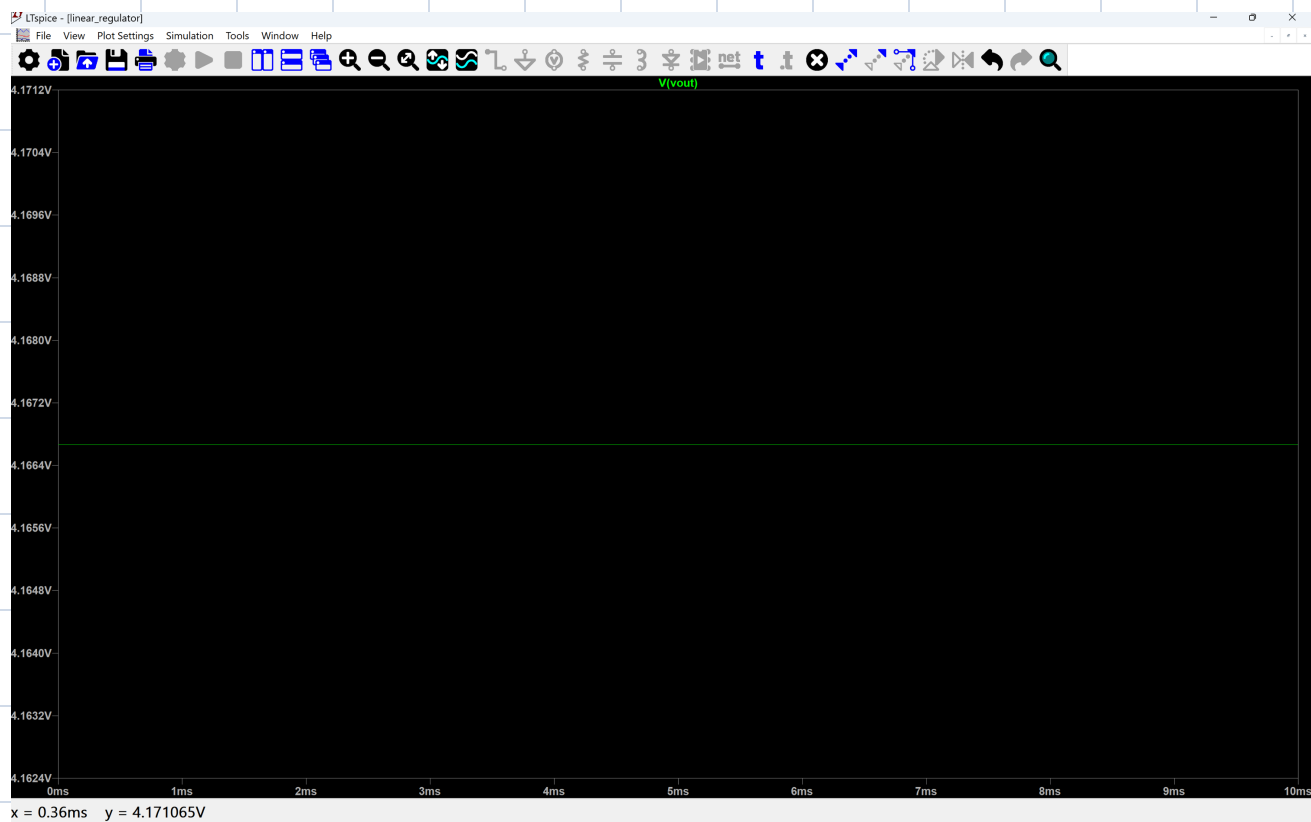

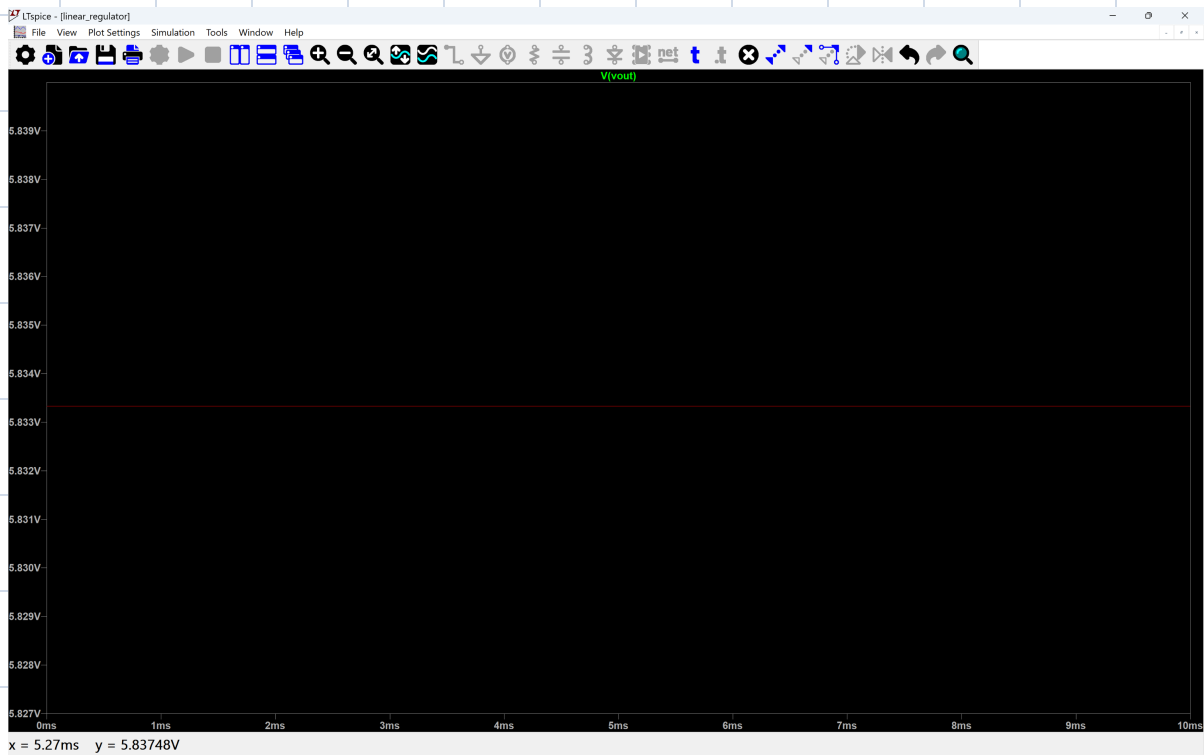

$V_{in} = 14V$
 $V_{out} = 5.833V$

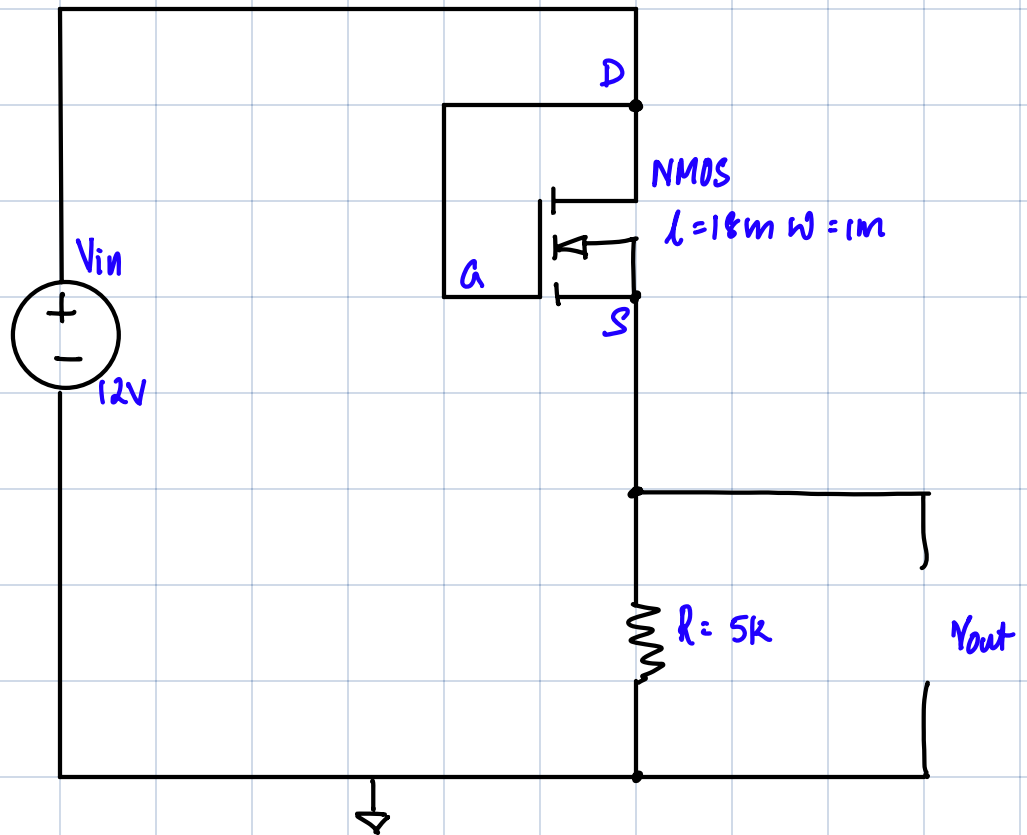Part II: Linear Regulator Using a MOSFET (n-mos4)



a)

Given: $V_{in} = 12V$
 $R = 5k\Omega$

NMOS:

a) $V_T = 1V$

b) $k'_n = 1mA/V^2$

c) $W = 1\mu m$

d) $L = 18\mu m$

To find V_{GS} , V_{DS} and V_{out}

Solution: Since the gate is shorted to the drain, $V_D = V_G$ [Short circuit current is zero, voltages at drain and gate are same.)

$$V_{GS} = V_G - V_S$$

$$V_{DS} = V_D - V_S$$

Since $V_{DS} = V_G - V_S$

$$\boxed{V_{DS} = V_{GS}}$$

Since R_1 and R_2 are connected in series the current through R_1 and R_2 are the same.

$\therefore I_D$ the drain current will be the same current through R_2 i.e. I_{R_2}

The voltage across resistor $R_2 = V_{out} = I_{R_2} R_2$

$$V_{out} = I_D R_2$$

$$I_D = \frac{V_{out}}{R_2}$$

$$\boxed{I_D = \frac{V_{out}}{5000}} \quad \therefore R_2 = 5k\Omega$$

We know that the drain current for a MOSFET is given by

$$I_D = \frac{k_n'}{2} \left(\frac{W}{L} \right) (V_{GS} - V_T)^2 \quad \rightarrow \textcircled{1}$$

Substituting $I_D = \frac{V_{out}}{5000}$

We know that according to KVL $V_{in} = V_{GS} + V_{out}$

$$V_{out} = V_{in} - V_{GS}$$

Substituting in $\textcircled{1}$

$$\frac{V_{in} - V_{GS}}{5000} = \frac{10^{-3}}{2} \times \frac{1}{18} (V_{GS} - 1)^2$$

Since $V_{GS} = V_{GS}$ $\therefore$ Drain and gate are shorted

$$12 - V_{DS} = \frac{5000 \times 10^{-3}}{2} \times \frac{1}{18} (V_{DS} - 1)^2$$

$$12 - V_{DS} = \frac{5}{36} (V_{DS} - 1)^2$$

$$432 - 36V_{DS} = 5(V_{DS}^2 + 1 - 2V_{DS})$$

$$432 - 36V_{DS} = 5V_{DS}^2 + 5 - 10V_{DS}$$

$$5V_{DS}^2 + 5 - 10V_{DS} - 432 + 36V_{DS} = 0$$

$$5V_{DS}^2 + 26V_{DS} - 427 = 0$$

$$\therefore V_{DS} = -\frac{61}{5}, 7$$

$$V_{DS} = 7V$$


Since

$$V_{GS} = V_{DS} = 7V$$


$$V_{out} = V_{in} - V_{DS}$$

$$= 12 - 7$$

$$V_{out} = 5V$$

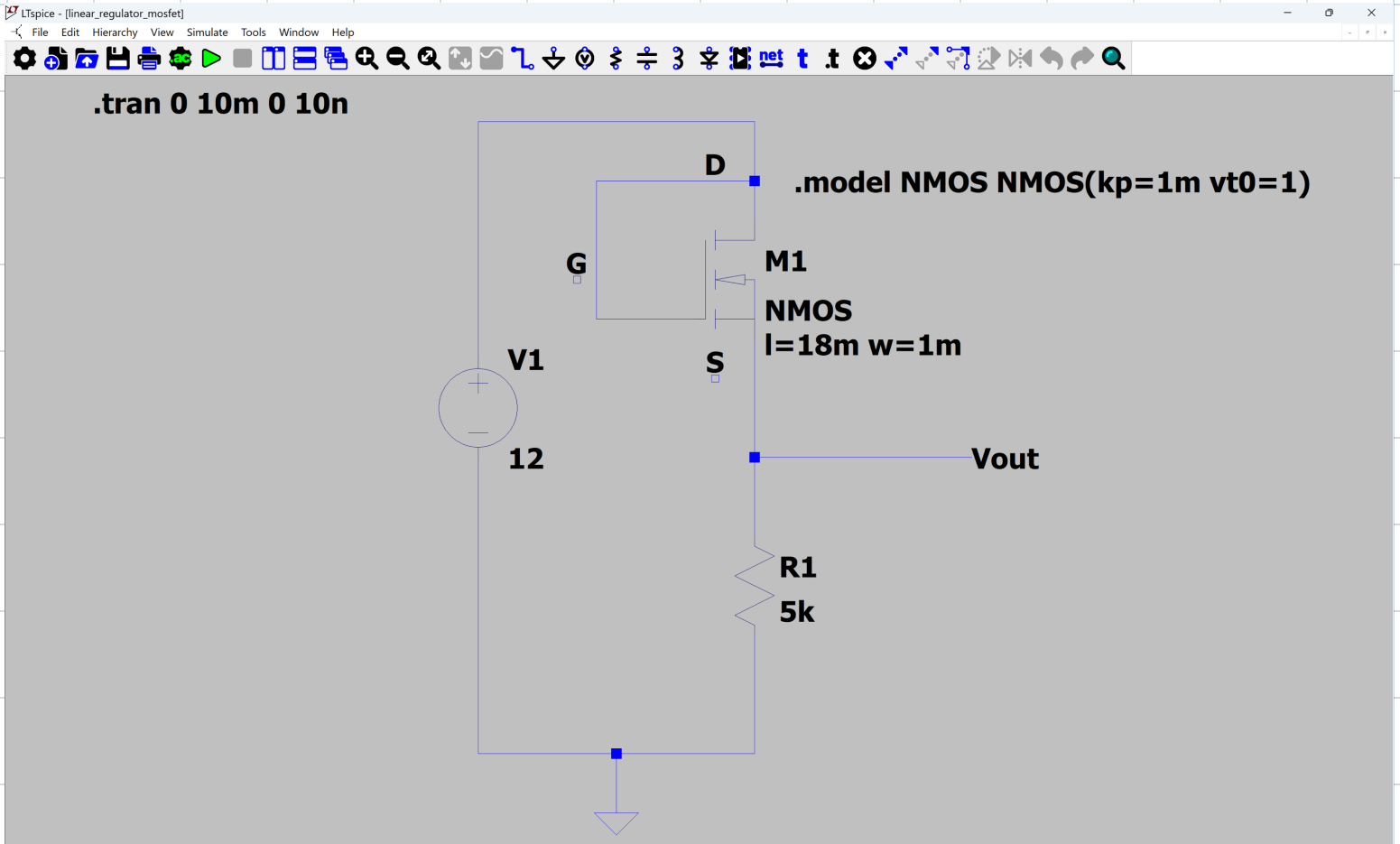


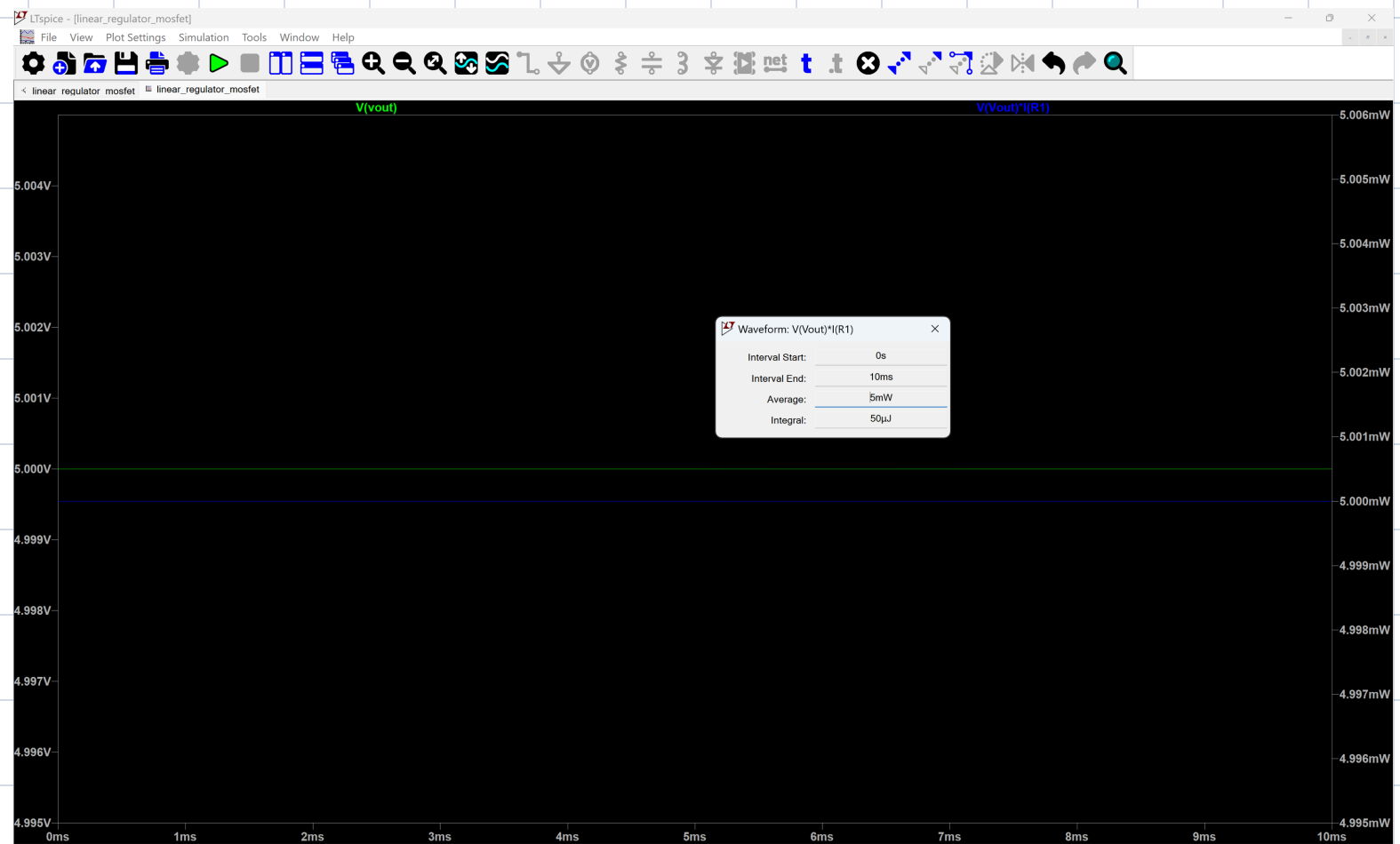
Right click to edit "l=18m w=1m", the Value2 of M1




Left-Click to redraw V(Vout)*I(R1)[W], Right-Click to edit. Control-Left-Click to integrate. Alt-Left-Click to reverse cross probe R1.


Question 3



i)

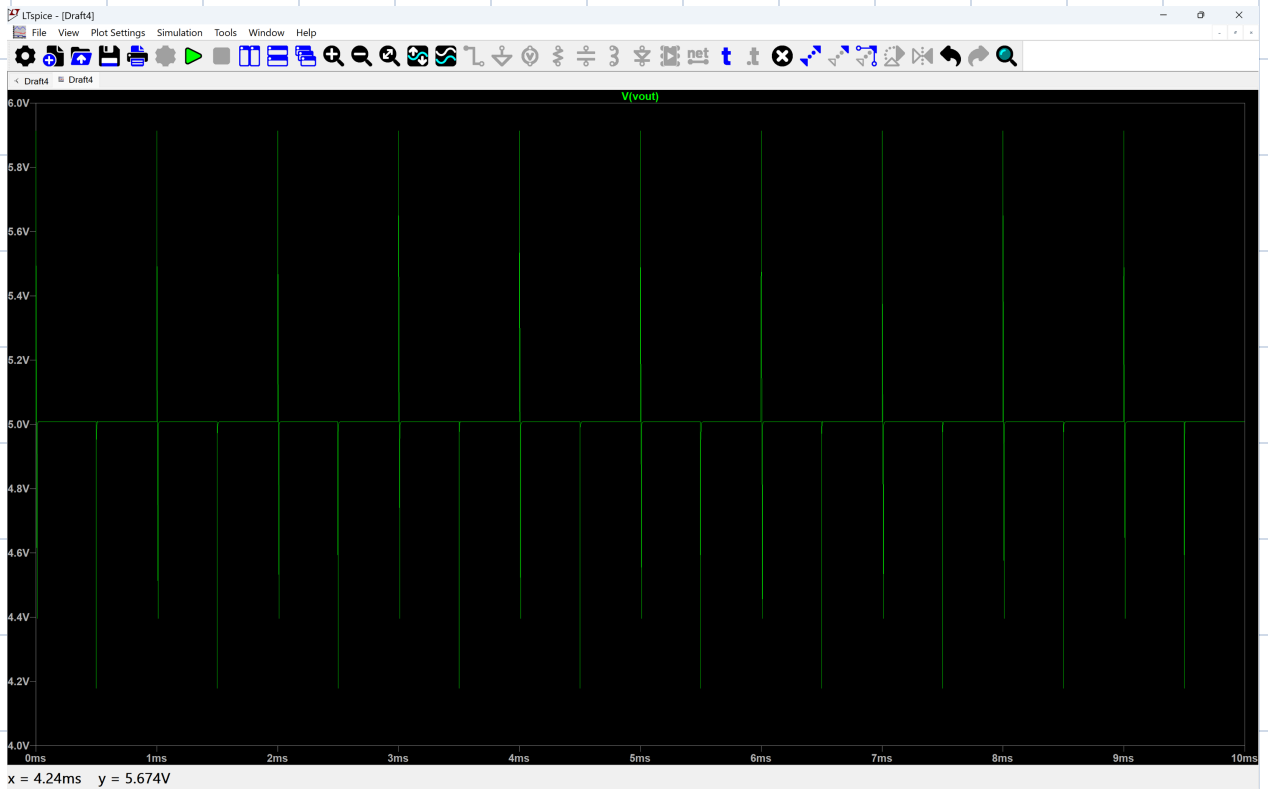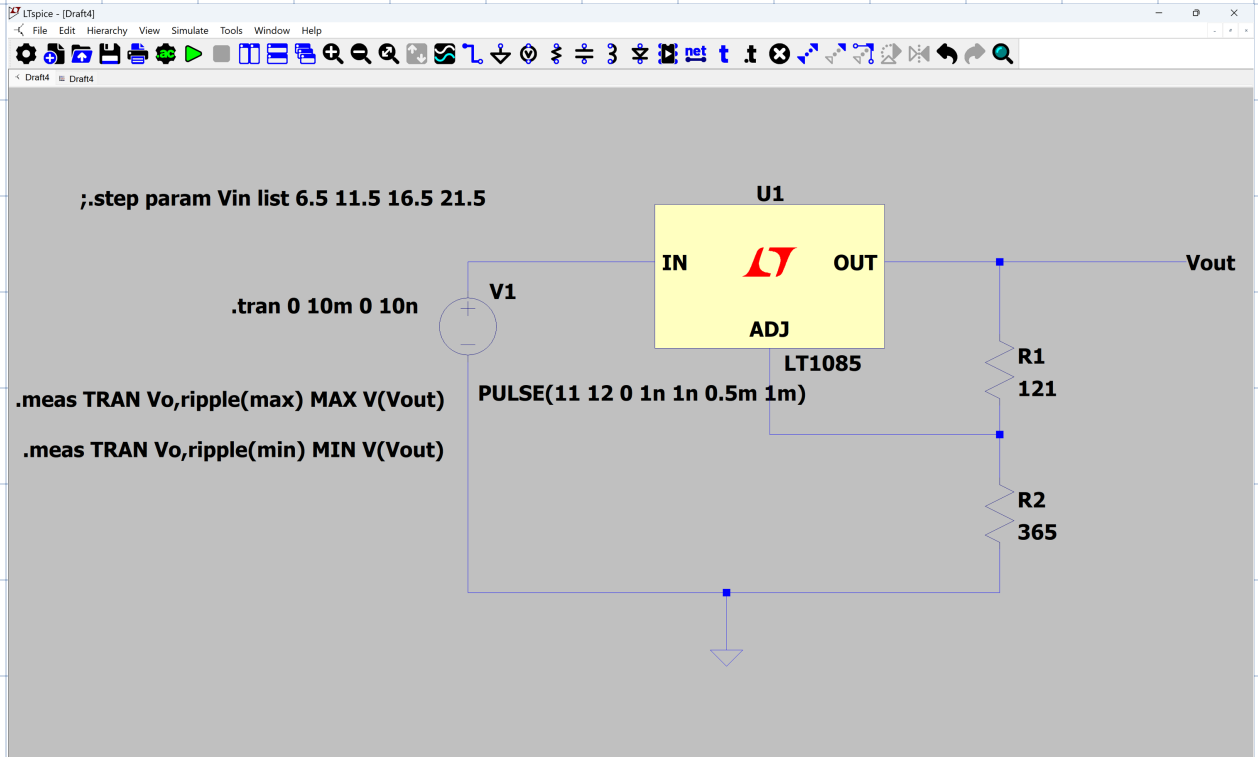

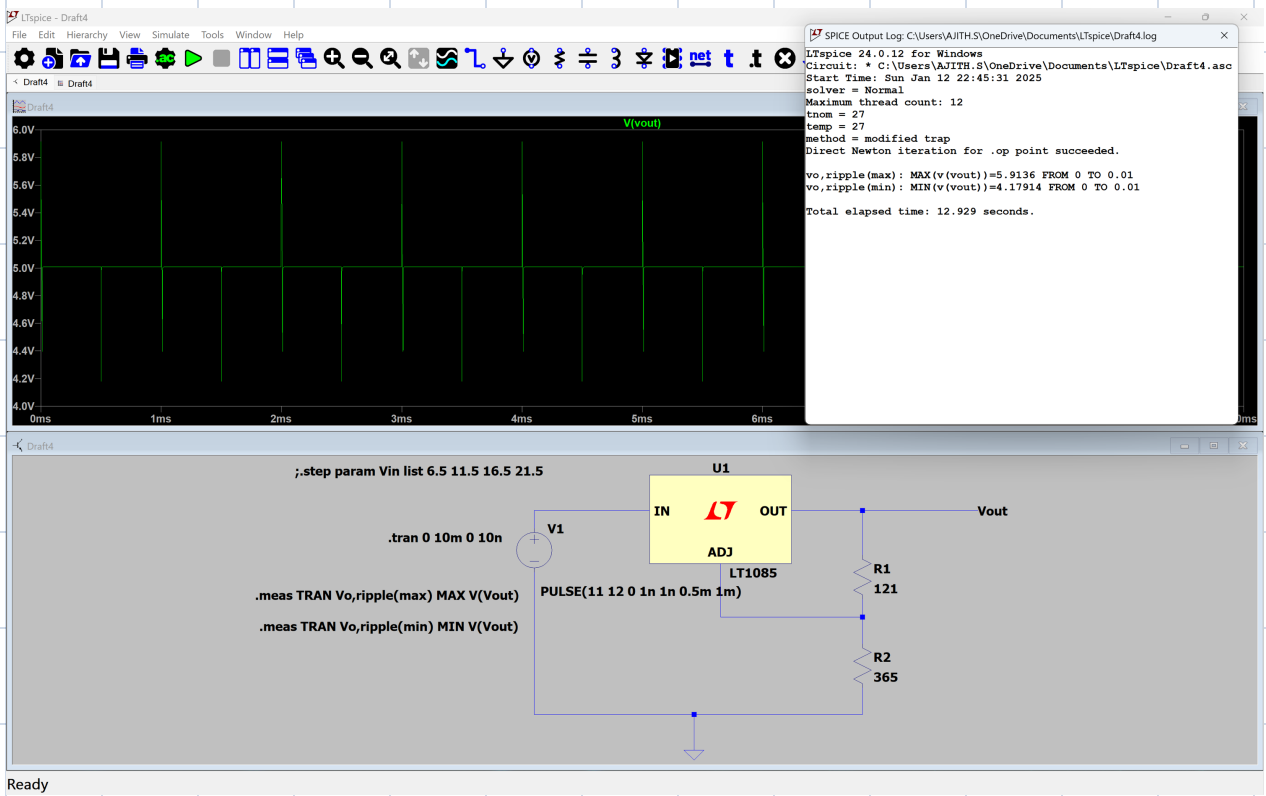

Output ripple max	5.9136 V
Output ripple min	4.17914 V
peak to peak values (max-min voltage)	1.73446 V

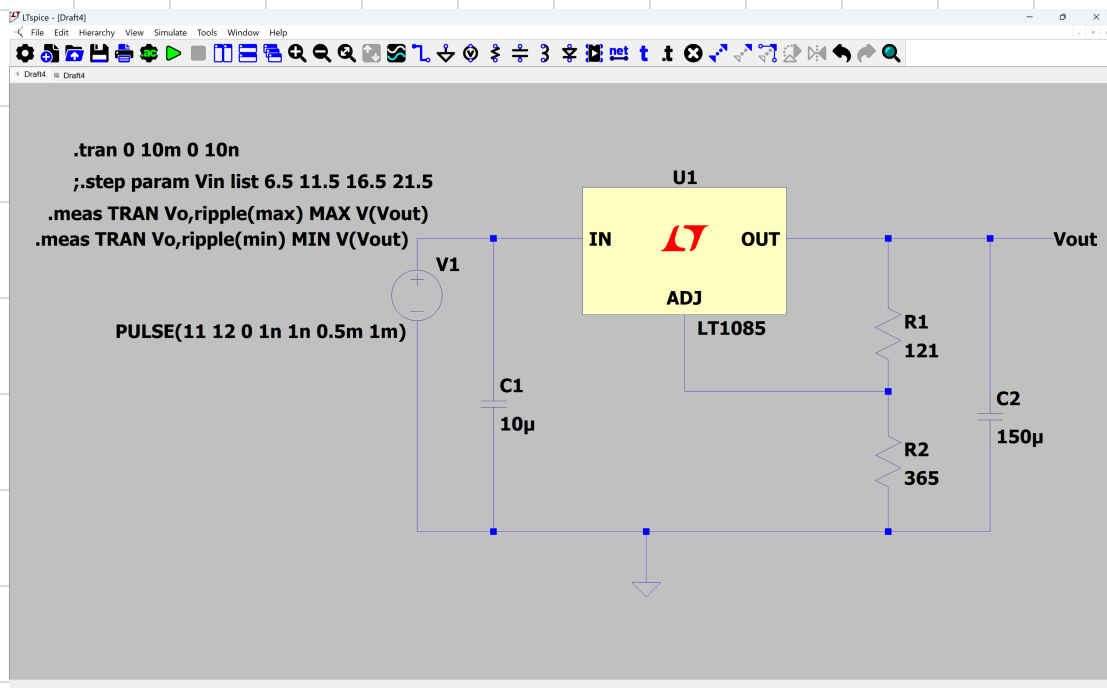

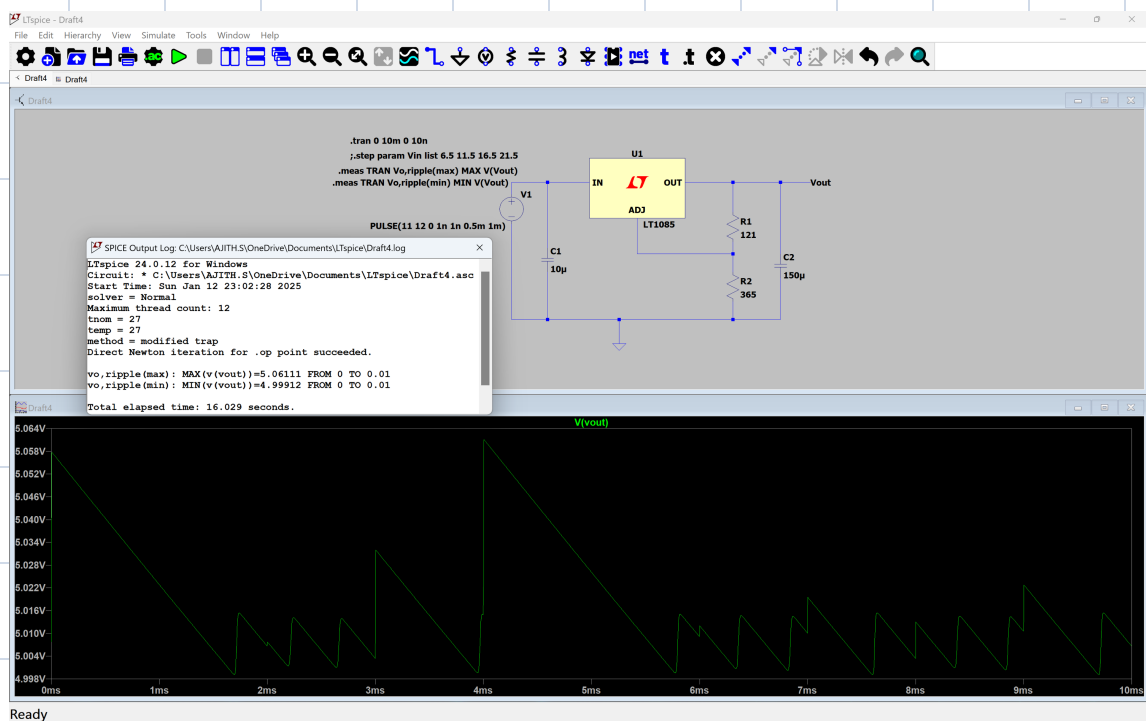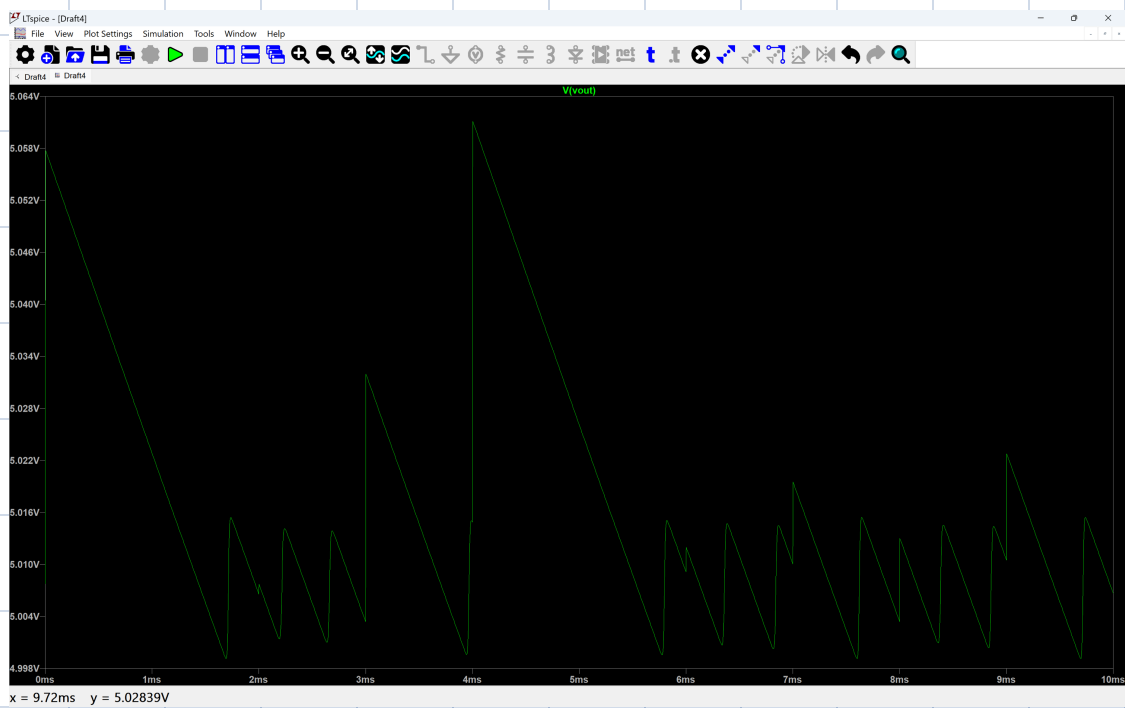

output ripple max	5.06111 V
output ripple min	4.99912V
peak to peak values(max-min voltage)	0.06199V

We can thus see that the Capacitor at the output reduces the peak to peak ripple from 1.73446V to 0.06199V.